



Pin 3 is Output
 This will drive the Current Regulator
 One 555 can power at least 10 Current
 Regulators.
 Jules Ryckebusch May 2017