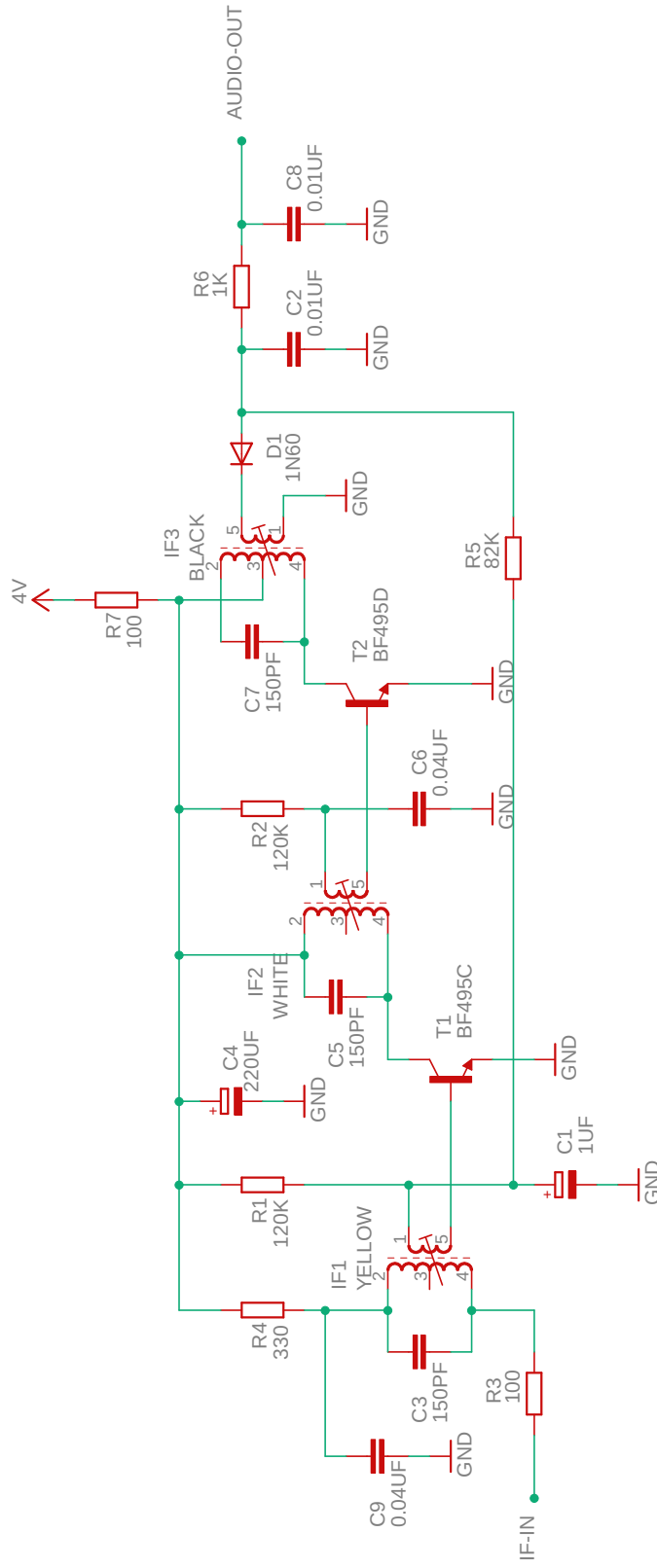


TWO STAGES IF AMPLIFIER



AUTODESK
EAGLE

Ramji Patel1376

TWO STAGES IF AMP.

8/4/2021 11:34 PM

Sheet: 1/1