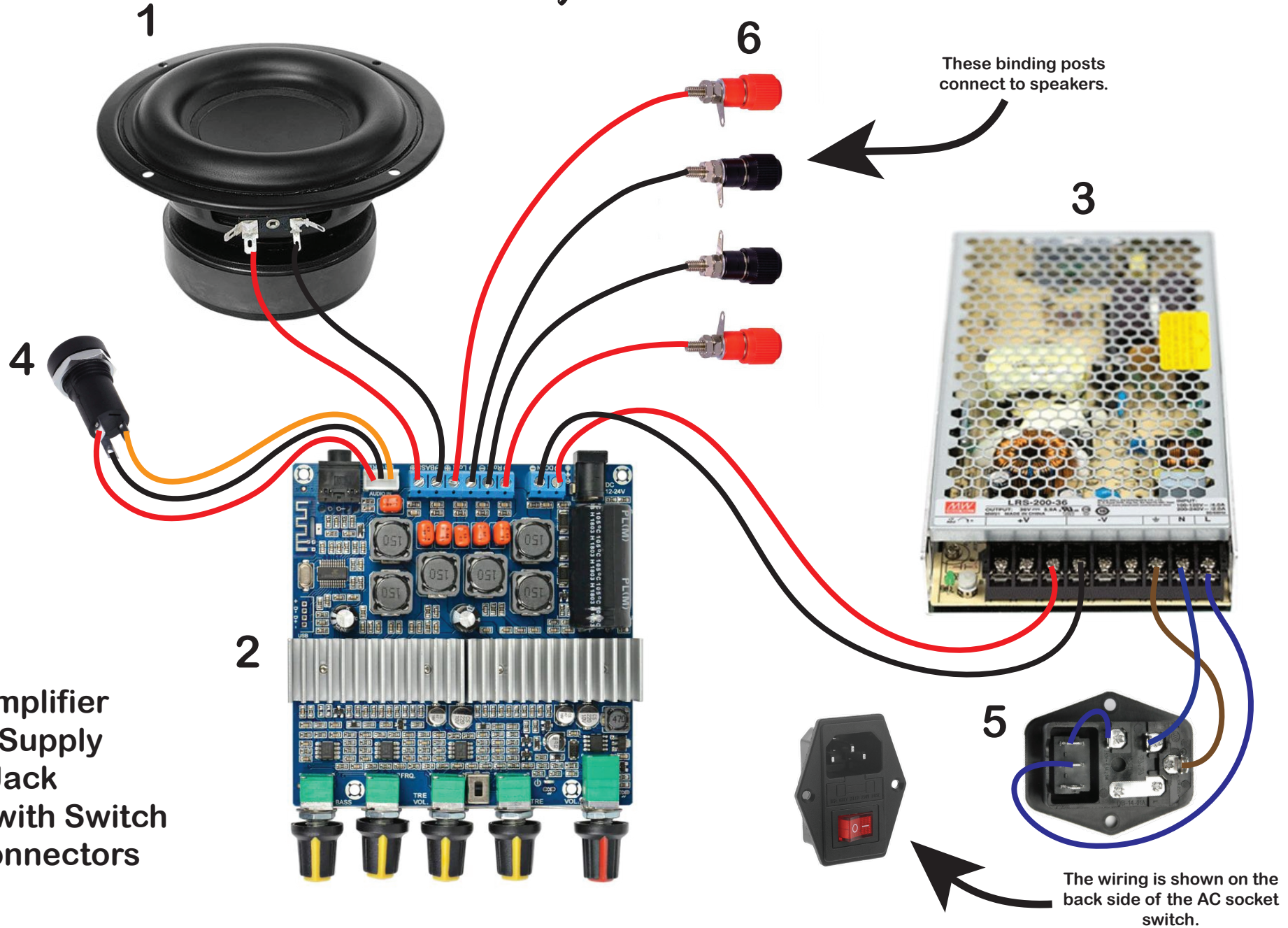


# Active Subwoofer Wiring Diagram

by *Donny Terek*



These binding posts connect to speakers.

- Parts list:**
- 1 - Woofer
  - 2 - TPA3116 Amplifier
  - 3 - 24V Power Supply
  - 4 - AUX Input Jack
  - 5 - AC Socket with Switch
  - 6 - Speaker Connectors

The wiring is shown on the back side of the AC socket switch.