



The led and buzzer represent their 12v counterparts. This build is for testing. No 12v and 3.3v power management TIP120 yet